

Assignment 5

IT451 : COA LAB

ANINDYA KUNDU

IT, 4th Semester

ID: 510817020 (Hx-19)


01-04-2019

Question 1

Design and simulate a 32 bit ALU with standard operations as given in Assignment II Q 5.

- a. Synthesize it for Spartan 6. Report device utilization.
- b. Synthesize the previously designed 16 bit ALU for the same device and report device utilization.
- c. Create appropriate test benches to reflect its functional behavior for all possible cases. Include the snapshots in your report.
- d. Prepare a comparative table between the two designs to reflect their difference in hardware complexities.

Unit	Function	Sel
Arithmetic	Transfer a	0000
	Increment a	0001
	Decrement a	0010
	Transfer b	0011
	Increment b	0100
	Decrement b	0101
	Add a and b	0110
	Add a and b with carry	0111
Logical	Complement a	1000
	Complement b	1001
	AND	1010
	OR	1011
	NAND	1100
	NOR	1101
	XOR	1110
	XNOR	1111

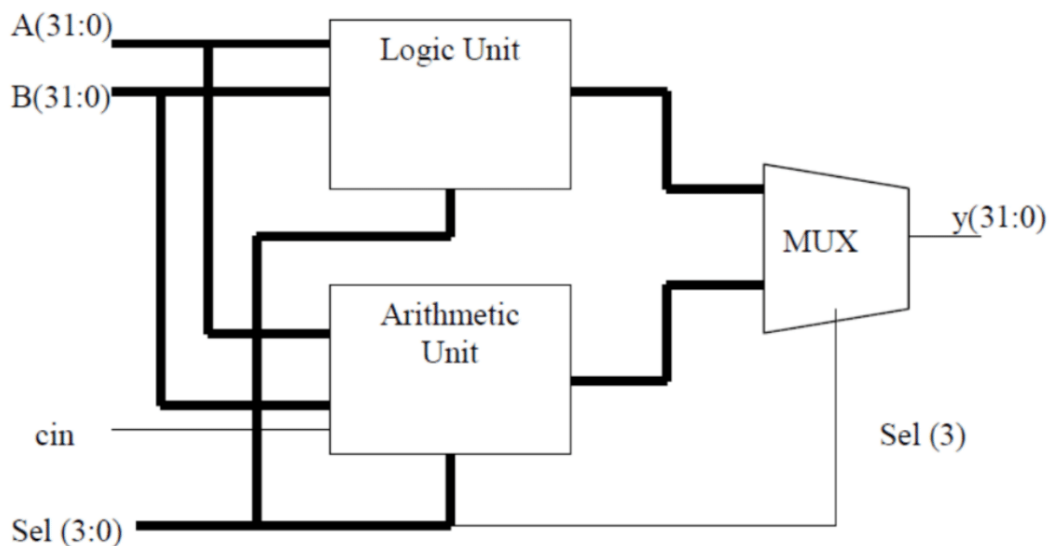

VHDL Module:

arithUnit.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity arithUnit is
    Port ( S : in      STD_LOGIC_VECTOR ( 3 downto 0);
          A : in      STD_LOGIC_VECTOR (31 downto 0);
          B : in      STD_LOGIC_VECTOR (31 downto 0);
          C : in      STD_LOGIC;
          Y : inout   STD_LOGIC_VECTOR (31 downto 0));
end arithUnit;

architecture Behavioral of arithUnit is

begin

process(S, A, B, C)
    variable uA, uB: unsigned(31 downto 0) := (others => '0');
begin
    uA := unsigned(A);
    uB := unsigned(B);

    if(S(3) = '0') then
        case S is
            when "0000" => Y <= A;
            when "0001" =>
                Y <= STD_LOGIC_VECTOR(uA + 1);
            when "0010" =>
                Y <= STD_LOGIC_VECTOR(uA - 1);
            when "0011" => Y <= B;
            when "0100" =>
                Y <= STD_LOGIC_VECTOR(uB + 1);
            when "0101" =>
                Y <= STD_LOGIC_VECTOR(uB - 1);
            when "0110" =>
                Y <= STD_LOGIC_VECTOR(uA + uB);
            when "0111" =>
                if(C = '1') then Y <= STD_LOGIC_VECTOR(uA + uB + 1);
                else
                    Y <= STD_LOGIC_VECTOR(uA + uB + 0);
                end if;
            when others => Y <= "00000000000000000000000000000000";
        end case;
    end if;
end process;

end Behavioral;
```

```

        end case;
    else Y <= "00000000000000000000000000000000";
    end if;
end process;

end Behavioral;

```

logicUnit.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity logicUnit is
    Port ( S : in          STD_LOGIC_VECTOR ( 3 downto 0);
          A : in          STD_LOGIC_VECTOR (31 downto 0);
          B : in          STD_LOGIC_VECTOR (31 downto 0);
          Y : inout       STD_LOGIC_VECTOR (31 downto 0));
end logicUnit;

architecture Behavioral of logicUnit is

begin

process(S, A, B, Y)
begin
    if(S(3) = '1') then
        case S is
            when "1000" => Y <= not A;
            when "1001" => Y <= not B;
            when "1010" => Y <= A and  B;
            when "1011" => Y <= A or   B;
            when "1100" => Y <= A nand B;
            when "1101" => Y <= A nor  B;
            when "1110" => Y <= A xor  B;
            when "1111" => Y <= A xnor B;
            when others => Y <= "00000000000000000000000000000000";
        end case;
    else Y <= "00000000000000000000000000000000";
    end if;
end process;

end Behavioral;

```

selMux.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity selMux is
    Port ( S : in  STD_LOGIC;
          P : in  STD_LOGIC_VECTOR (31 downto 0);
          Q : in  STD_LOGIC_VECTOR (31 downto 0);
          Y : out STD_LOGIC_VECTOR (31 downto 0));
end selMux;

architecture Behavioral of selMux is

begin
    Y <= P when S = '0' else Q;
end Behavioral;
```

ALU.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ALU is
    Port ( A : in  STD_LOGIC_VECTOR (31 downto 0);
          B : in  STD_LOGIC_VECTOR (31 downto 0);
          C : in  STD_LOGIC;
          S : in  STD_LOGIC_VECTOR ( 3 downto 0);
          Y : out STD_LOGIC_VECTOR (31 downto 0));
end ALU;


architecture Structural of ALU is
    signal M, N, O : STD_LOGIC_VECTOR (31 downto 0);

begin

    AU : entity work.arithUnit port map(S, A, B, C, M);
    LU : entity work.logicUnit port map(S, A, B, N);
    MX : entity work.selMux      port map(S(3), M, N, Y);

end Structural;
```

RTL Schematic:

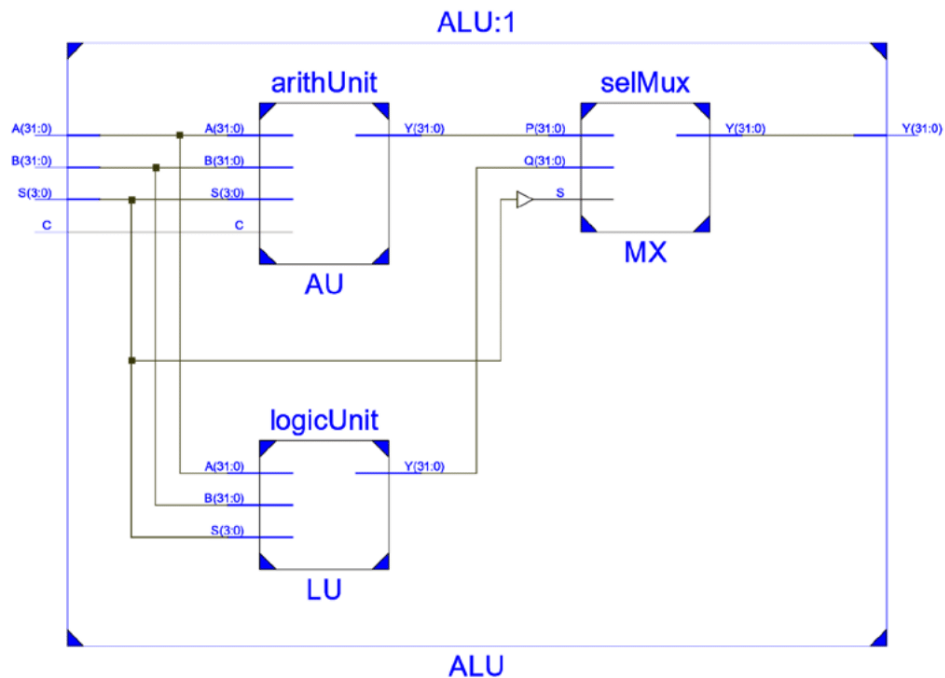

VHDL Test Bench: *tb_ALU.vhd*

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE ieee.numeric_std.ALL;
```

```
ENTITY tb_ALU IS  
END tb_ALU;
```

```
ARCHITECTURE behavior OF tb_ALU IS
```

```
    COMPONENT ALU
```

```
        PORT ( A : in  STD_LOGIC_VECTOR (31 downto 0);  
              B : in  STD_LOGIC_VECTOR (31 downto 0);  
              C : in  STD_LOGIC;  
              S : in  STD_LOGIC_VECTOR ( 3 downto 0);  
              Y : out STD_LOGIC_VECTOR (31 downto 0));
```

```
    END COMPONENT;
```

```
    SIGNAL a : STD_LOGIC_VECTOR (31 downto 0) := (others => '0');  
    SIGNAL b : STD_LOGIC_VECTOR (31 downto 0) := (others => '0');  
    SIGNAL c : STD_LOGIC := '0';  
    SIGNAL s : STD_LOGIC_VECTOR ( 3 downto 0) := (others => '0');  
    SIGNAL y : STD_LOGIC_VECTOR (31 downto 0);
```

```
BEGIN
```

```
    uut: ALU PORT MAP(  
        A => a,  
        B => b,  
        C => c,  
        S => s,  
        Y => y
```


```

    A => a,
    B => b,
    C => c,
    S => s,
    Y => y
);

process
begin
    a <= "00000000110000000101001010111010";
    b <= "000000000000010101001001011011011";
    c <= '1';
    s <= "0000";
    while s >= "0000" loop
        wait for 100ns;
        s <= STD_LOGIC_VECTOR(unsigned(s) + 1);
    end loop;
    wait;
end process;
END;

```

Simulation:

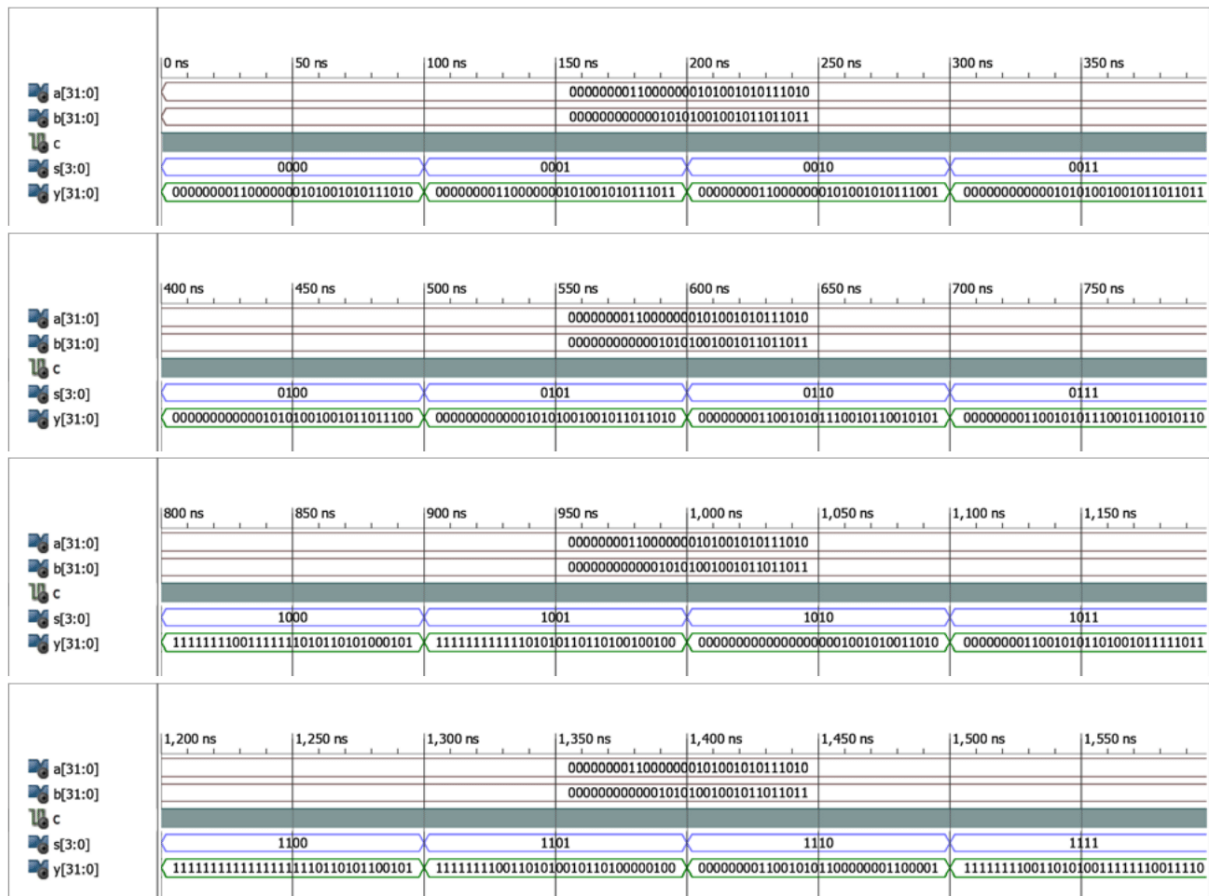

Device Utilisation Summary:

32-bit ALU

Device Utilization Summary (estimated values)			[-]
Logic Utilization	Used	Available	Utilization
Number of Slice LUTs	384	27288	1%
Number of fully used LUT-FF pairs	0	384	0%
Number of bonded IOBs	101	296	34%

16-bit ALU

Device Utilization Summary (estimated values)			[-]
Logic Utilization	Used	Available	Utilization
Number of Slice LUTs	192	27288	0%
Number of fully used LUT-FF pairs	0	192	0%
Number of bonded IOBs	53	296	17%

Hardware Complexity Comparison:

32-bit ALU

16-bit ALU

Slice Logic Utilization	Used	Available	Utilization	Used	Available	Utilization
Number of Slice Registers	0	54,576	0%	0	54,576	0%
Number of Slice LUTs	384	27,288	1%	192	27,288	1%
Number used as logic	381	27,288	1%	189	27,288	1%
Number using O6 output only	226			114		
Number using O5 output only	92			44		
Number using O5 and O6	63			31		
Number used as ROM	0			0		
Number used as Memory	0	6,408	0%	0	6,408	0%
Number used exclusively as route-thrus	3			3		
Number with same-slice register load	0			0		
Number with same-slice carry load	3			3		
Number with other load	0			0		
Number of occupied Slices	119	6,822	1%	67	6,822	1%
Number of MUXCYs used	192	13,644	1%	96	13,644	1%
Number of LUT Flip Flop pairs used	384			192		
Number with an unused Flip Flop	384	384	100%	192	192	100%
Number with an unused LUT	0	384	0%	0	192	0%
Number of fully used LUT-FF pairs	0	384	0%	0	192	0%
Number of slice register sites lost to control set restrictions	0	54,576	0%	0	54,576	0%
Number of bonded IOBs	101	296	34%	53	296	17%