

Assignment 3

IT451 : COA LAB

ANINDYA KUNDU

IT, 4th Semester

ID: 510817020 (Hx-19)

25-03-2019

Question 1

Design the following types of code converters in a single module using switch case statement.

- a. Binary to Gray
- b. Gray to Binary
- c. Binary to Excess-3
- d. Excess-3 to Binary

VHDL Module: *mod_codeConv.vhd*

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity mod_codeConv is
    Port ( s1 : in  STD_LOGIC_VECTOR (1 downto 0);
          ip : in  STD_LOGIC_VECTOR (3 downto 0);
          op : out STD_LOGIC_VECTOR (3 downto 0));
end mod_codeConv;

architecture Dataflow of mod_codeConv is
    signal s : STD_LOGIC_VECTOR (3 downto 0);


begin

    process(s1, ip)
    begin
        case s1 is
            when "00" =>
                s(3) <= ip(3);
                s(2) <= ip(3) xor ip(2);
                s(1) <= ip(2) xor ip(1);
                s(0) <= ip(1) xor ip(0);
            when "01" =>
                s(3) <= ip(3);
                s(2) <= ip(2) xor ip(3);
                s(1) <= ip(1) xor ip(2) xor ip(3);
                s(0) <= ip(0) xor s(1) xor ip(2) xor ip(3);
            when "10" =>
                s <= STD_LOGIC_VECTOR (unsigned(ip) + 3);
            when "11" =>
                s <= STD_LOGIC_VECTOR (unsigned(ip) - 3);
            when others =>
                end case;
        end process;
    end process;
```

```
op <= s;
```

```
end Dataflow;
```

RTL Schematic:

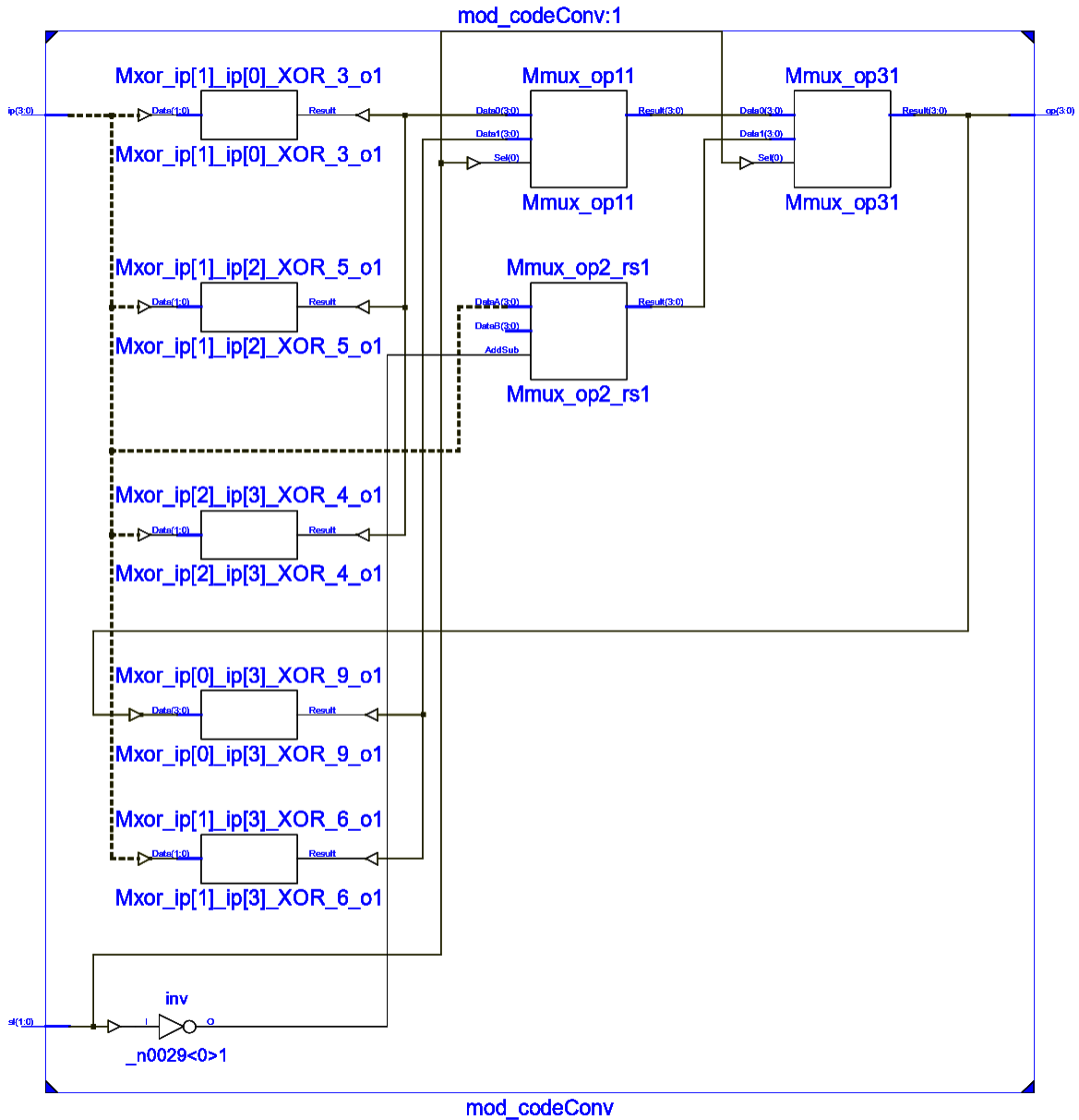

VHDL Test Bench: *tb_codeConv.vhd*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_codeConv IS
END tb_codeConv;

ARCHITECTURE behavior OF tb_codeConv IS
    COMPONENT mod_codeConv
    PORT(
        sl : IN  std_logic_vector(1 downto 0);
        ip : IN  std_logic_vector(3 downto 0);
        op : OUT std_logic_vector(3 downto 0)
    );
    END COMPONENT;


    signal sl : std_logic_vector(1 downto 0) := (others => '0');
    signal ip : std_logic_vector(3 downto 0) := (others => '0');

    signal op : std_logic_vector(3 downto 0);

BEGIN
    uut: mod_codeConv PORT MAP (
        sl => sl,
        ip => ip,
        op => op
    );

    stim_proc: process
    begin
        sl <= "00", "01" after 250 ns, "10" after 500 ns, "11" after 750ns;
        ip <= "0110"; wait for 125ns; ip <= "1100"; wait for 125ns;
        ip <= "0101"; wait for 125ns; ip <= "1010"; wait for 125ns;
        ip <= "0000"; wait for 125ns; ip <= "1001"; wait for 125ns;
        ip <= "0011"; wait for 125ns; ip <= "1100"; wait for 125ns;
        wait;
    end process;
END;
```

Simulation:

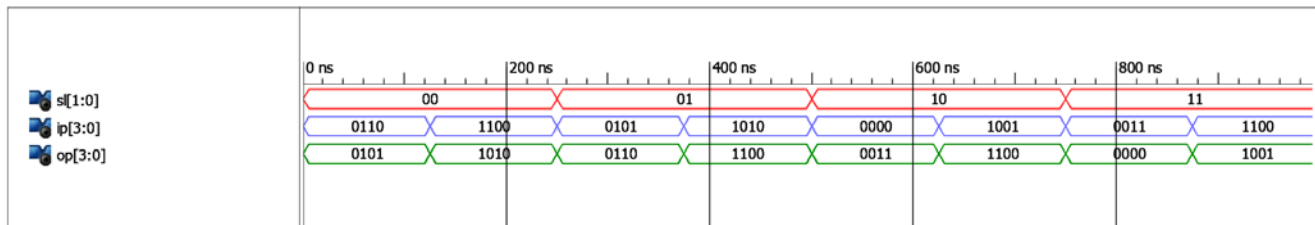

Question 2

Design and simulate 8 bit unsigned binary multiplier. Synthesize it for Spartan 6. Report device utilization.

VHDL Module: *mod_unsignedMultiplier.vhd*


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity mod_unsignedMultiplier is
    Port ( a : in  STD_LOGIC_VECTOR (7 downto 0);
          b : in  STD_LOGIC_VECTOR (7 downto 0);
          y : out STD_LOGIC_VECTOR (15 downto 0));
end mod_unsignedMultiplier;


architecture Behavioral of mod_unsignedMultiplier is

begin
    y <= STD_LOGIC_VECTOR(unsigned(a) * unsigned(b));
end Behavioral;
```

RTL Schematic:

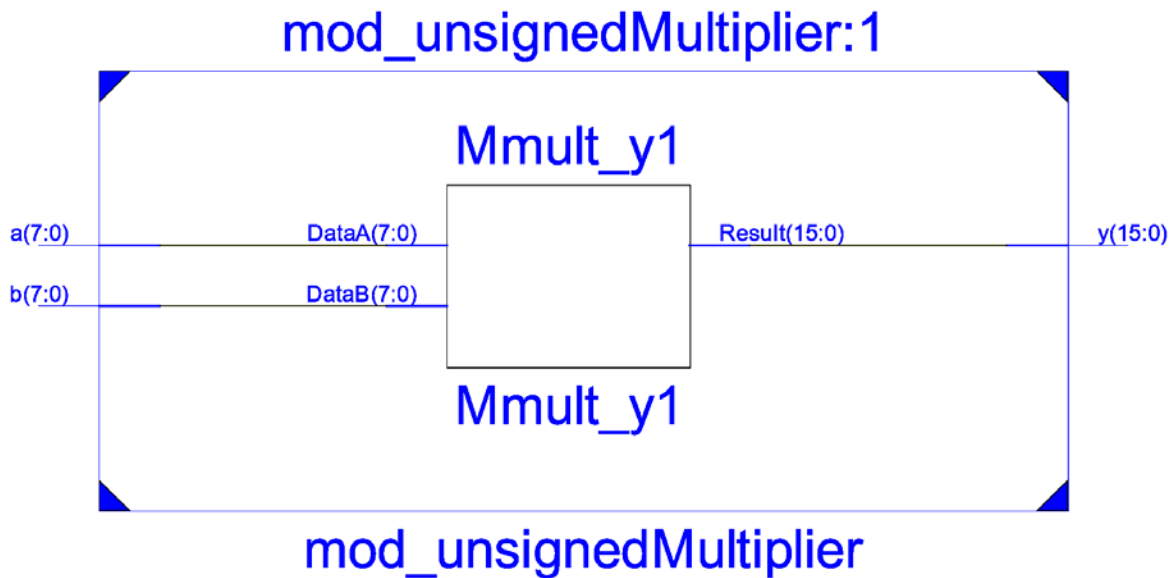

Device Utilisation Summary:

Device Utilization Summary (estimated values)				
Logic Utilization	Used	Available	Utilization	
Number of bonded IOBs	32	296	10%	
Number of DSP48A1s	1	58	1%	

VHDL Test Bench: *tb_unsignedMultiplier.vhd*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_unsignedMultiplier IS
END tb_unsignedMultiplier;

ARCHITECTURE behavior OF tb_unsignedMultiplier IS
    COMPONENT mod_unsignedMultiplier
    PORT(
        a : IN  std_logic_vector(7 downto 0);
        b : IN  std_logic_vector(7 downto 0);
        y : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    signal a : std_logic_vector(7 downto 0) := (others => '0');
    signal b : std_logic_vector(7 downto 0) := (others => '0');
    signal y : std_logic_vector(15 downto 0);

BEGIN
    uut: mod_unsignedMultiplier PORT MAP (
        a => a,
        b => b,
        y => y
    );

    proc_a: process
    begin
        a <= "00001111", "11110001" after 250 ns, "10101010" after 500 ns, "01010101"
        after 750 ns;
        wait;
    end process;


    proc_b: process
    begin
        b <= "00110011", "11110000" after 250 ns, "11001100" after 500 ns, "10010011"
        after 750 ns;
```

```

wait;
end process;
END;

```

Simulation:

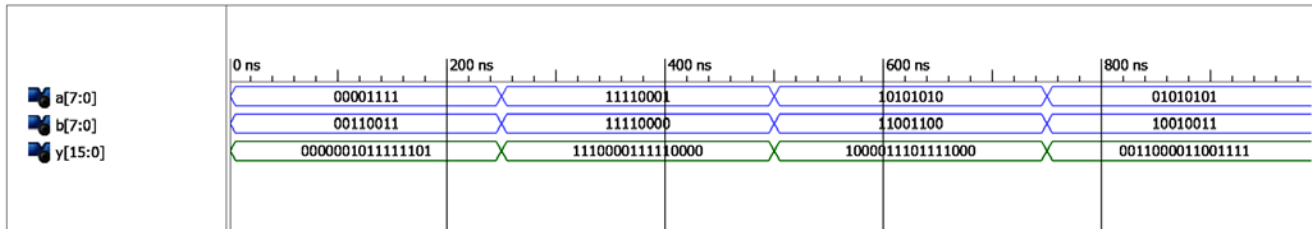

Question 3

Design and simulate a 32 bit divider. Synthesize it for Spartan 6. Report device utilization.

VHDL Module: *mod_signedDivider.vhd*

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity mod_unsignedDivider is
    Port ( a : in  STD_LOGIC_VECTOR (3 downto 0);
          b : in  STD_LOGIC_VECTOR (3 downto 0);
          q : out STD_LOGIC_VECTOR (3 downto 0);
          r : out STD_LOGIC_VECTOR (3 downto 0));
end mod_unsignedDivider;

architecture Behavioral of mod_unsignedDivider is
    signal au, bu, qu, ru : signed (3 downto 0);

begin

    process (a, b) is
        variable cnt  : STD_LOGIC_VECTOR (31 downto 0);
        variable tem  : STD_LOGIC_VECTOR (31 downto 0);


    begin
        cnt  := "00000000000000000000000000000000";
        tem  := a;

        while (tem >= b and cnt < "11111111111111111111111111111111") loop
            tem  := STD_LOGIC_VECTOR(signed(tem) - signed(b));
            cnt  := STD_LOGIC_VECTOR(signed(cnt) + 1);
        end loop;

        q <= cnt;
        r <= tem;
    end process;

end Behavioral;
```

RTL Schematic:

 

Device Utilisation Summary:

Device Utilization Summary (estimated values)				
Logic Utilization	Used	Available	Utilization	
Number of Slice LUTs	1247	27288		4%
Number of fully used LUT-FF pairs	0	1247		0%
Number of bonded IOBs	128	296		43%

VHDL Test Bench: *tb_signedDivider.vhd*

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_unsignedDivider IS
END tb_unsignedDivider;

ARCHITECTURE behavior OF tb_unsignedDivider IS
    COMPONENT mod_unsignedDivider
    PORT(
        a : IN  std_logic_vector(3 downto 0);
        b : IN  std_logic_vector(3 downto 0);
        q : OUT std_logic_vector(3 downto 0);
        r : OUT std_logic_vector(3 downto 0)
    );
    END COMPONENT;

    signal a : std_logic_vector(3 downto 0) := (others => '0');
    signal b : std_logic_vector(3 downto 0) := (others => '0');
    signal q : std_logic_vector(3 downto 0);
    signal r : std_logic_vector(3 downto 0);

BEGIN
    uut: mod_unsignedDivider PORT MAP (
        a => a,
        b => b,
        q => q,
        r => r
    );

```

```
proc_a: process
begin
    a <= "00000000000000000000000000000000111";
    wait for 333 ns;
    a <= "11110000111111110000111100000011";
    wait for 333 ns;
    a <= "00000000000000000000111111111001000";
    wait;
end process;
```

```
proc_b: process
begin
    b <= "00000000000000000000000000000010";
    wait for 333 ns;
    b <= "11110000111111110000111100000011";
    wait for 333 ns;
    b <= "11000000000000000000000000000001";
    wait;
end process;
END;
```

Simulation:

